


# Lab1 Fibonacci number detector

## Design Process

The main idea is use K-map to construct SOP, and use verilog to implement it.


Since Fibonacci numbers in range  $[0, 15]$  are: 0, 1, 2, 3, 5, 8, 13, so I write down some 1 in the corresponding block in K-map.

K-map

 

$$A'B' + BC'D + B'C'D'$$

Circuit

 

So now we know the result is equal to  $A'B' + BC'D + B'C'D'$ .

For **Gate Level Description**, we need to use some logic gates to implement the circuit.

Since the not operation can be replace with  $\sim$ , so here I didn't use `not not0()` to get Not.

From K-map we can figure out we have three Products, so I create `a0`, `a1`, `a2`, and in the end sum them up will get the result.

```

module Fib_G(in, out);
    input [3:0] in;
    output out;

    wire a0, a1, a2;

    and and0(a0, ~in[3], ~in[2]);
    and and1(a1, in[2], ~in[1], in[0]);
    and and2(a2, ~in[2], ~in[1], ~in[0]);

    or or0(out, a0, a1, a2);
endmodule

```

For *Dataflow Description*, we could just write the whole logical operation in single line, just like what tutorial says.

```

module Fib_D(in, out);
    input [3:0] in;
    output out;

    assign out = (!in[3] & !in[2]) | (in[2] & !in[1] & in[0]) | (!in[2] & !in[1] & !in[0]);
endmodule

```

For *Behavior Description*, we could directly write the numbers that should output **1** in the code, when receive these values, let output be **1**, otherwise **0**.

```

module Fib_B(in, out);
    input [3:0] in;
    output out;
    reg out;

    always@(*) begin
        case(in)
            0, 1, 2, 3, 5, 8, 13: out = 1'b1;
            default: out = 1'b0;
        endcase
    end
endmodule

```

# Execution Result

I wrote a testbranch like this:

```
module Fib_tb;
    parameter delay = 100;

    wire out_G, out_D, out_B;
    reg [3:0] in;

    wire isFib;
    assign isFib = in == 0 || in == 1 || in == 2 || in == 3 || in == 5 || in == 8 || in ==
13;


    initial begin
        in = 0;
        repeat (16) begin
            #delay
            $display("in = %2d\tout_G = %1b\tout_D = %1b\tout_B = %1b", in, out_G,
out_D, out_B);
            if((isFib && (out_G & out_D & out_B) == 0) || (!isFib && (out_G | out_D
| out_B) == 1))
                begin
                    $display("Wrong Answer!");
                    $finish;
                end
            in = in + 1;
        end
        $display("\t=====");
        $display("\t| Accepted! |");
        $display("\t=====");
        $finish;
    end

    Fib_G FG(in, out_G);
    Fib_D FD(in, out_D);
    Fib_B FB(in, out_B);

endmodule
```

I directly write the correct fibonacci numbers in testbranch, and for every output check whether they are the same as the answer.

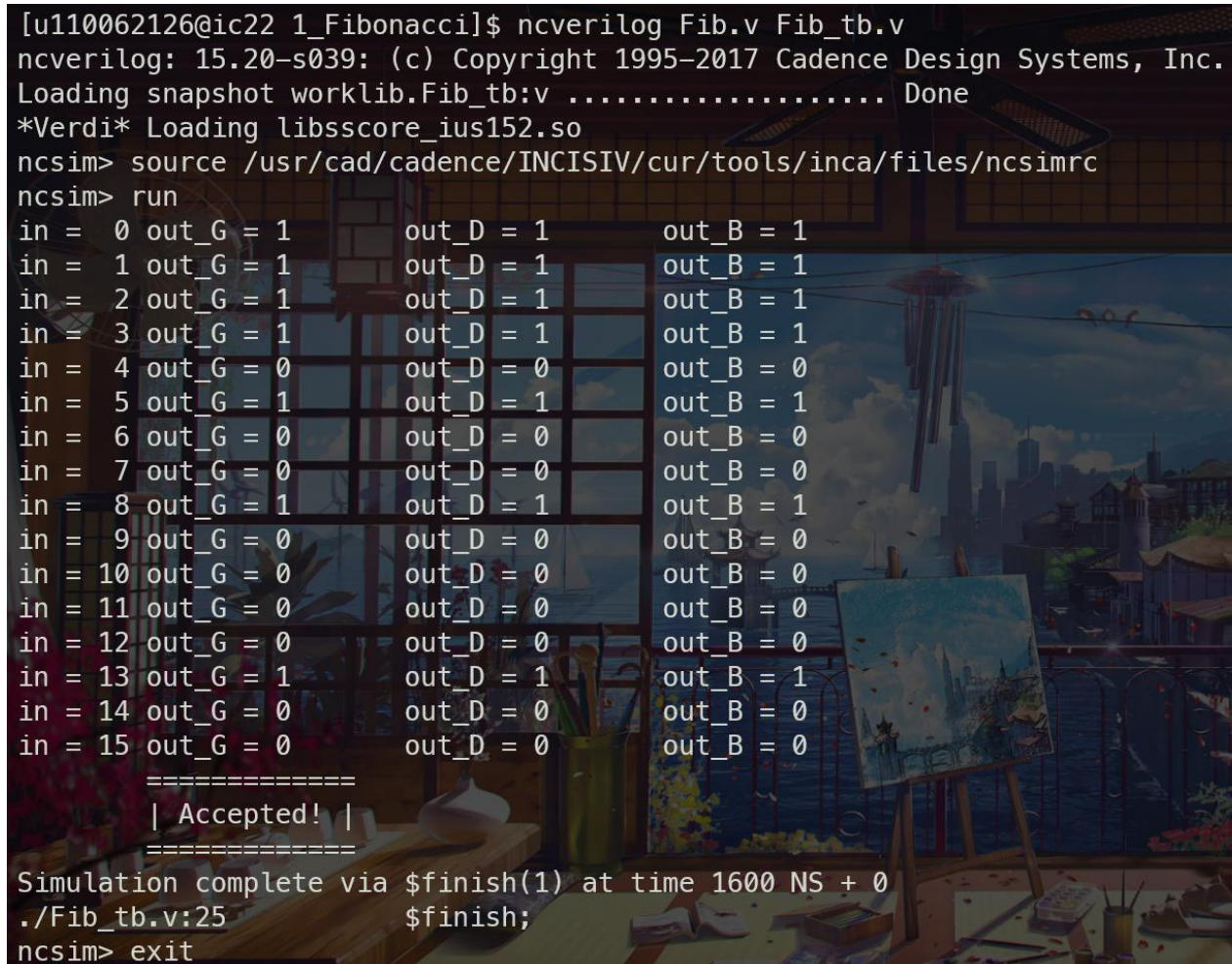If there's wrong answer, it'll output **Wrong Answer!**, otherwise **Accepted!**



```
[u110062126@ic22 1_Fibonacci]$ ncverilog Fib.v Fib_tb.v
ncverilog: 15.20-s039: (c) Copyright 1995-2017 Cadence Design Systems, Inc.
Loading snapshot worklib.Fib_tb.v ..... Done
*Verdi* Loading libsscore_ius152.so
ncsim> source /usr/cad/cadence/INCISIV/cur/tools/inca/files/ncsimrc
ncsim> run
in = 0 out_G = 1      out_D = 1      out_B = 1
in = 1 out_G = 1      out_D = 1      out_B = 1
in = 2 out_G = 1      out_D = 1      out_B = 1
in = 3 out_G = 1      out_D = 1      out_B = 1
in = 4 out_G = 0      out_D = 0      out_B = 0
in = 5 out_G = 1      out_D = 1      out_B = 1
in = 6 out_G = 0      out_D = 0      out_B = 0
in = 7 out_G = 0      out_D = 0      out_B = 0
in = 8 out_G = 1      out_D = 1      out_B = 1
in = 9 out_G = 0      out_D = 0      out_B = 0
in = 10 out_G = 0      out_D = 0      out_B = 0
in = 11 out_G = 0      out_D = 0      out_B = 0
in = 12 out_G = 0      out_D = 0      out_B = 0
in = 13 out_G = 1      out_D = 1      out_B = 1
in = 14 out_G = 0      out_D = 0      out_B = 0
in = 15 out_G = 0      out_D = 0      out_B = 0

=====
| Accepted! |
=====
Simulation complete via $finish(1) at time 1600 NS + 0
./Fib_tb.v:25      $finish;
ncsim> exit
```

## The problem I faced

The main problem I faced is I accidentally type some wrong syntax, just use the error message to debug and find the solution on websites.

## What I've learned in this Lab

From this lab, I first implement a logic circuit in verilog by myself, I know

- How to use input and output
- How to use **and**, **or**, **not** logic gates
- Difference between **~** and **!** in verilog
- Difference between **wire** and **reg**
- How to write a testbranch